

Lesson 7- Circuit Experiments

Date:

Question(s):

How does length of wire in a circuit affect brightness of the bulb? How does number of batteries in a circuit affect brightness of the bulb? How does number of bulbs affect the brightness of the bulbs?

Prediction:

Materials:

Procedures:

Data/Observations:

Independent variable:	Trial 1	Trial 2	Trial 3

Conclusion:

Turn the question or prediction/hypothesis into a statement to be used as a topic sentence. Support your topic sentence with 2 or 3 supporting statements.